



DEPARTMENT OF ELECTRONIC SYSTEMS

TFE4152 DESIGN OF INTEGRATED CIRCUITS

---

# Project Report

---

*Authors:*

Brage Gaasø Samsonsen and Niklas Strømsnes

18th February 2021

---

## Abstract

The purpose of this project is to design and implement the analog part of a digital camera controlled by a digital control logic. This is done by calculating the parameters of the needed components, such as transistor dimensions and the capacitance of the capacitors. The analog circuit will be implemented in the circuit simulation program AIM-Spice. The digital control logic will be implemented using Verilog in Active HDL. The purpose of the analog circuit is to capture light and send out an output signal based on the lights strength. The digital control logic's purpose is to send the needed control signals to the analog circuit so that it can capture the light and create the desired output signal. We end up with a fully functional analog circuit with the correct digital control signals sent from the digital control logic.

---

# Contents

<b>List of Figures</b>	<b>iii</b>
<b>List of Tables</b>	<b>iii</b>
<b>1 Introduction</b>	<b>1</b>
<b>2 Theory</b>	<b>2</b>
2.1 Analog Circuit . . . . .	2
2.1.1 Transistor dimensions . . . . .	4
2.1.2 Capacitor values . . . . .	7
2.2 Digital part . . . . .	8
<b>3 Realization</b>	<b>12</b>
3.1 Parameters . . . . .	12
3.1.1 Body effect parameters . . . . .	12
3.1.2 Transistor parameters . . . . .	12
3.1.3 Capacitor parameters . . . . .	12
3.1.4 Parameters summary . . . . .	13
3.2 Analog circuitry . . . . .	13
3.3 Digital circuitry . . . . .	15
<b>4 Conclusion</b>	<b>17</b>
<b>Bibliography</b>	<b>18</b>
<b>Appendix</b>	<b>19</b>
A AIM-Spice code . . . . .	19
B Verilog code . . . . .	21
C Verilog test bench . . . . .	25

---

## List of Figures

1	Overview of the system. . . . .	1
2	Overview of the pixel circuit [Larsen 2020]. . . . .	2
3	Overview of the 2x2 analog camera circuit. . . . .	3
4	Overview the active load. . . . .	4
5	Overview of the timing diagram. . . . .	8
6	Overview of the FSM. . . . .	9
7	Overview of the block diagram for RE_Control . . . . .	10
8	Overview of the block diagram for the entire camera circuit, composed of a <b>Pulse_shaper</b> , the <b>RE_Control</b> and the <b>Pixel_electronics</b> . We are not going to design the <b>Puls_shaper</b> . . . . .	11
9	The voltages of the signals <i>Expose</i> , <i>Erase</i> , <i>NRE_R1</i> , <i>NRE_R2</i> , the here identical output signals, and the voltage over $C_S$ . . . . .	14
10	The voltages of the signals simulated with slow corners. . . . .	14
11	The voltages of the signals simulated with fast corners. . . . .	15
12	Overview of the timing simulated control signals. . . . .	15
13	Overview of the timing diagram when decreasing time. . . . .	15
14	Overview of the timing diagram when resetting the signal. . . . .	16

## List of Tables

1	Table of transistor and capacitor parameters. . . . .	13
---	---	----

---

# 1 Introduction

We are going to design a digital camera using a specific circuit-topology. The digital camera will be composed of an analog and a digital part. To do this, we are going to use a circuit modeling program where we can design our analog circuit. We are also going to use a Hardware Description Language (HDL) to design and simulate the digital part of the camera circuit. The whole system will be composed as shown in Figure 1. The system will first receive an analog signal. This signal will be picked up by the analog sensor. It will then be converted to a digital signal using an analog to digital converter (ADC). All the sub-systems are being controlled by a Digital Control Logic (DCL). We will not be designing the ADC or anything coming after it.

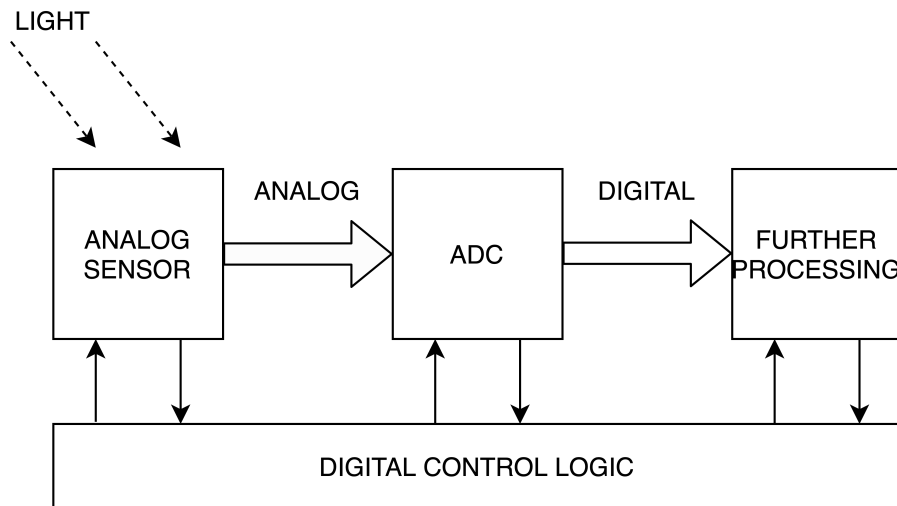


Figure 1: Overview of the system.

---

## 2 Theory

The whole camera is composed of an analog and a digital part. We will start off by designing the analog circuitry and then move on to the digital circuitry and logic. We also have to determine the dimensions of all the transistors and the values of the capacitors capacitance to make the analog circuit work as intended.

### 2.1 Analog Circuit

We have to start designing a circuit to detect light and turn it into an analog voltage. We will therefore design the pixel circuit shown in Figure 2.

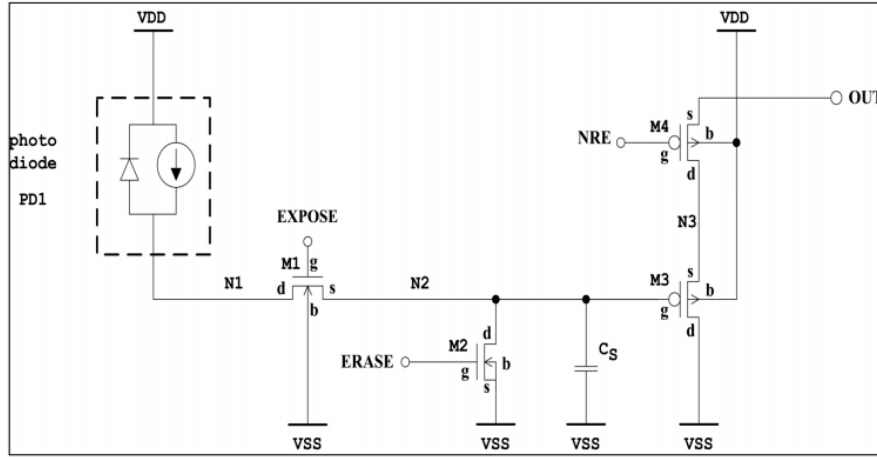


Figure 2: Overview of the pixel circuit [Larsen 2020].

On the left side of the circuit, we have the photo diode  $PD1$ . The strength of the light hitting the diode determines how strong the current will be. When the signal  $EXPOSE$  is high, the transistor  $M1$  is active and the current from the photo diode will charge the capacitor  $C_S$ . To get an output signal at  $OUT$ , the transistor  $M4$  has to be active. Since this transistor is active low, it will be active when the read signal  $NRE$  is low and deactivates when  $NRE$  is high. As long as  $C_S$  is charged, the transistor  $M3$  will not activate and the output signal will be affected by the gate voltage and not be grounded to  $VSS$ .  $M3$  is also an active low transistor, hence it will not be active when  $C_S$  is charged. If  $M2$  activates, the capacitor will discharge, since both sides of the capacitor will be grounded to  $VSS$ . This will happen when the signal  $ERASE$  is high.  $M1$ ,  $M2$  and  $M4$  will therefore act as switches.  $M3$  will act as an active load.

The pixel circuit is a subcircuit of a larger circuit, shown in Figure 3. This is the analog camera circuit and it is composed of several subcircuits.

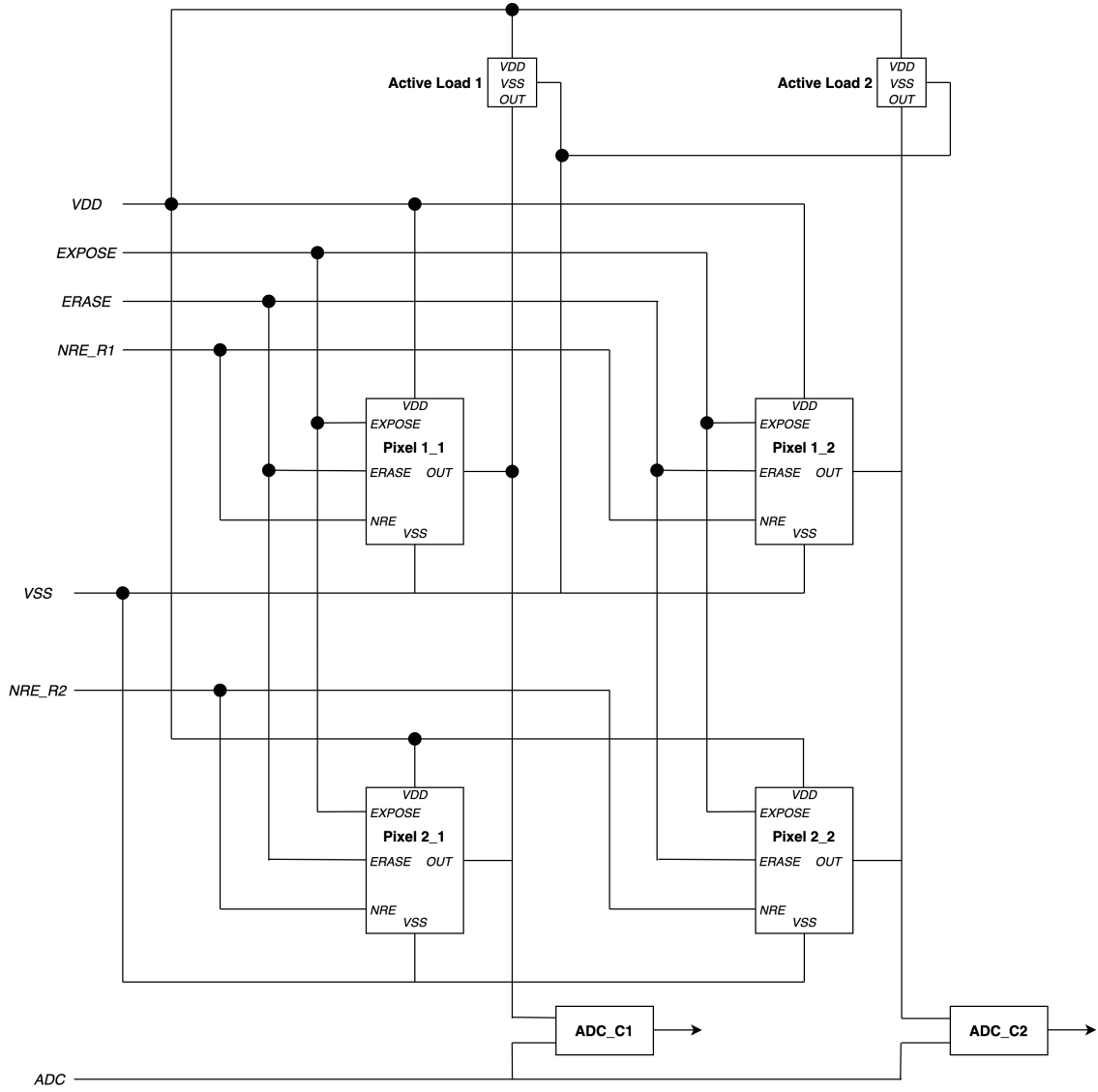


Figure 3: Overview of the 2x2 analog camera circuit.

The pixel circuit shown in Figure 2 is represented by the four boxes in Figure 3, **Pixel 1\_1**, **Pixel 1\_2**, **Pixel 2\_1** and **Pixel 2\_2**. These four boxes are individual pixel circuit. The analog camera circuit is composed of two columns, each of them composed of two pixel circuits, an analog to digital converter and an active load. The analog to digital converters are represented by the bottom two boxes, **ADC\_C1** and **ADC\_C2**. The active loads are represented by the top two boxes, **Active load 1** and **Active load 2**. Column 1 is composed of **Pixel 1\_1**, **Pixel 1\_2**, **ADC\_C1** and **Active load 1**. Column 2 is composed of **Pixel 2\_1**, **Pixel 2\_2**, **ADC\_C2** and **Active load 2**. The inputs of the camera circuit are similar to the inputs of the pixel circuit, being *EXPOSE*, *ERASE*, *VDD*, *VSS*, as well as the read signals for each row *NRE\_R1* and *NRE\_R2*. These input signals are connected to their pixel circuit equivalents. *NRE\_R1* is connected to **Pixel 1\_1** and **Pixel 1\_2** *NRE* and *NRE\_R2* is connected to **Pixel 2\_1** and **Pixel 2\_2** *NRE*. The reason why we have divided our main analog circuit into two columns is so that we can get two *OUT* signals from two read signals instead of four. The *OUT* signals from the pixel circuits are then sent to the analog to digital converters to be further processed digitally. The *OUT* signals are also connected to an active load, shown as the two smaller boxes in the top of the figure. These active loads are better shown and described in Figure 4.

 


Figure 4: Overview the active load.

The active loads are composed of the PMOS transistor  $MC$  and the capacitor  $C_C$ . These circuits have three inputs, being  $VDD$ ,  $VSS$  and the  $OUT$  signal from the pixel circuits. By including an active load at each output, we stabilize the  $OUT$  signals, and if the current through  $M4$  is high when  $NRE$  is active, we get the functionality of a buffer circuit between  $M3$ ,  $M4$ ,  $MC$  and  $C_C$ . This is wanted, as we want a linear relationship between the current controlled by the photo diode and the voltage at  $OUT$ .

### 2.1.1 Transistor dimensions

In total, there are 18 different transistors in our analog circuit, however many of them have the same functions and can have similar dimensions. This means that all the  $M1$  transistors in the different pixel circuits can share the same dimensions. Having this in mind, we only have to determine the dimensions of five different transistors, being  $M1$ ,  $M2$ ,  $M3$  and  $M4$  from the pixel circuits, and  $MC$  from the active loads.

All the transistor dimensions have to be between the predetermined limits

$$L_{min} < L < L_{max} \quad (1)$$

and

$$W_{min} < W < W_{max} \quad (2)$$

When deciding the parameters, we also have to keep in mind that the body effect might affect the threshold voltages of our transistors. The body effect will change the threshold voltage of a given transistor depending on its source-bulk voltage  $V_{SB}$ , surface potential  $\phi_F$ , the body effect constant  $\gamma$  and the zero substrate bias voltage  $V_{T0}$ . The threshold voltage  $V_{TN}$  is then given by

$$V_{TN} = V_{TN0} + \gamma(\sqrt{|V_{SB} - 2\phi|} - \sqrt{|2\phi_F|}), \quad (3)$$



---

where the surface potential is given by

$$2\phi_F = 2 \left( \frac{kT}{q} \right) \ln \left( \frac{N_A}{n_i} \right) \quad (4)$$

By looking at the surface potential, we can conclude that it will remain constant as long as we don't change the temperature  $T$  or the doping concentration  $N_A$ . The intrinsic carrier concentration  $n_i$ , the elementary charge  $q$ , and Boltzmann constant  $k$  are all constants. For an NMOS transistor that has its bulk connected to ground and not in the same node as its source, an increase in source-bulk voltage will decrease the threshold voltage. For a PMOS transistor however, that has its bulk connected to  $VDD$ , an increase in source-bulk voltage will increase the threshold voltage. Note that because of this,  $M2$  a threshold voltage equal to  $V_{TN0}$ , and both  $M3$  and  $M4$  will have a higher threshold voltage. It is possible to neglect the body effect if the doping concentration is low enough, resulting in a threshold voltage almost equal to the zero substrate bias voltage.

The body effect can be neglected if the factor  $\gamma$ , given by

$$\gamma = \frac{\sqrt{2qN_aK_s\epsilon_0}}{C_{ox}}, \quad (5)$$

is small. Here,  $K_s$  is the relative permittivity of the semiconductor substrate. The gate capacitance  $C_{ox}$  depends on the relative permittivity  $K_{ox}$  and the thickness  $t_{ox}$  of the oxide layer at the gate, in the relation

$$C_{ox} = \frac{K_{ox}\epsilon_0}{t_{ox}} \quad (6)$$

To determine the dimensions of the transistors, we have to know that the leakage current  $I_{D(off)}$  is given by

$$I_{D(off)} \approx I_{D0} \left( \frac{W}{L} \right) e^{q(-V_S - V_{TN})/(nkT)}, \quad (7)$$

where  $n$  is the relation

$$n = \frac{C_{ox} + C_{j0}}{C_{ox}} \quad (8)$$

and the current  $I_{D0}$  is given by

$$I_{D0} = (n - 1)\mu_n C_{ox} \left( \frac{kT}{q} \right)^2 \quad (9)$$

By knowing this, we can minimize the leakage current by adjusting the width and the length of the transistor. By selecting a larger value for the length than the width, we get a low leakage current. When determining the parameters for  $M1$  and  $M2$ , we know that if the leakage in the transistors are too significant, the capacitor  $C_S$  will never be fully charged, which is not ideal since it will result in inaccurate readings. We will therefore have to make the width of  $M1$  and  $M2$  minimal, and the lengths maximal to minimize the leakage current.

To determine the dimensions of the three PMOS transistors  $M3$ ,  $M4$  and  $MC$ , we have to look at the drain current  $I_D$  in saturation given by

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{eff})^2, \quad (10)$$

---

where  $V_{eff}$  is given by difference between the gate-source voltage  $V_{GS}$  and  $V_{TN}$

$$V_{eff} = V_{GS} - V_{TN} \quad (11)$$

To get the largest possible drain current, we will have to make the width of the transistor much larger than the length of the transistor. For  $M3$  and  $MC$  we use that their effective voltages  $V_{eff}$  are given by

$$V_{eff,M3} = V_{OUT} - V_{N2} - V_{TN} \quad (12)$$

$$V_{eff,MC} = V_{DD} - V_{OUT} - V_{TN} \quad (13)$$

$V_{OUT}$  is the output voltage,  $V_{N2}$  is the voltage in the node  $N2$  which is also the gate voltage for  $M3$  as well as being the same voltage as  $V_{CS}$ .  $V_{CS}$  is the voltage of the capacitor  $C_S$ .  $V_{DD}$  is the supply voltage of the entire circuit. We want the transistors to operate in the saturation region which gives us the following inequalities

$$V_{TN} \leq V_{OUT} - V_{N2} \quad (14)$$

$$V_{TN} \leq V_{DD} - V_{OUT} \quad (15)$$

Since the two transistors have the same drain current  $I_D$ , we can get the following equations by using (7), (12) and (13)

$$\frac{\mu_n C_{ox}}{2} \frac{W_{M3}}{L_{M3}} (V_{eff,M3})^2 = \frac{\mu_n C_{ox}}{2} \frac{W_{MC}}{L_{MC}} (V_{eff,MC})^2 \quad (16)$$

which we can simplify to

$$\frac{W_{M3}}{L_{M3}} (V_{eff,M3})^2 = \frac{W_{MC}}{L_{MC}} (V_{eff,MC})^2 \quad (17)$$

By squaring 17, we get

$$\sqrt{\frac{W_{M3}}{L_{M3}}} V_{eff,M3} = \sqrt{\frac{W_{MC}}{L_{MC}}} V_{eff,MC} \quad (18)$$

By inserting (12) and (13) into (18) we get

$$\sqrt{\frac{W_{M3}}{L_{M3}}} (V_{OUT} - V_{N2} - V_{TN}) = \sqrt{\frac{W_{MC}}{L_{MC}}} (V_{DD} - V_{OUT} - V_{TN}) \quad (19)$$

By solving (19) for the output voltage  $V_{OUT}$ , we get

$$V_{OUT} = \frac{\sqrt{\frac{W_{M3}}{L_{M3}}}}{\sqrt{\frac{W_{M3}}{L_{M3}}} + \sqrt{\frac{W_{MC}}{L_{MC}}}} V_{N2} + \frac{\sqrt{\frac{W_{MC}}{L_{MC}}}}{\sqrt{\frac{W_{M3}}{L_{M3}}} + \sqrt{\frac{W_{MC}}{L_{MC}}}} V_{DD} + \frac{\sqrt{\frac{W_{M3}}{L_{M3}}} - \sqrt{\frac{W_{MC}}{L_{MC}}}}{\sqrt{\frac{W_{M3}}{L_{M3}}} + \sqrt{\frac{W_{MC}}{L_{MC}}}} V_{TN} \quad (20)$$

To maximize the gain of the output voltage  $V_{OUT}$ , we have to make the fraction in front of  $V_{N2}$  and  $V_{TN}$  as large as possible and the fraction in front of  $V_{DD}$  as low as possible. This is because

---

we don't want to let  $V_{DD}$  interfere with the output voltage. This is possible by making the width of  $M3$  as long as possible and the length as short as possible, as well as making the width of  $MC$  as short as possible and the length as long as possible. We want  $M4$  to affect the buffer circuit as little as possible. We will therefore have to make the resistance in the transistor as low as we can by making the current through it as high as possible. This is achieved by maximizing the width and minimizing the length of  $M4$ .

### 2.1.2 Capacitor values

There are six capacitors in our main analog circuit: one in each pixel circuit and one in each active load. The capacitances in the active loads **Active load 1** and **Active load 2** are predetermined. We will only have to determine the four capacitors in the pixel circuits and they will all share the same capacitance. These four capacitors are represented as  $C_S$ , with their own individual pixel circuit. Their capacitances are decided to be within the constraint

$$C_S \leq C_{max} \quad (21)$$

We know that the voltage  $V_{CS}$  over the capacitors is given by

$$V_{CS} = \frac{1}{C_S} \int_0^t I(\tau) d\tau, \quad (22)$$

where  $t$  is the expose time for the capacitors to charge up, and  $I(\tau)$  is the current charging the capacitors.  $I(\tau)$  and  $t$  are given the restrictions

$$I_{min} \leq I(\tau) \leq I_{max} \quad (23)$$

and

$$t_{min} \leq t \leq t_{max} \quad (24)$$

Assuming that  $I(\tau)$  is a direct current, we get

$$V_{CS} = \frac{It}{C_S} \quad (25)$$

from the integral, which then gives us the expression

$$C_S = \frac{It}{V_{CS}} \quad (26)$$

for the capacitance.

We can find the minimum value of the capacitors  $C_{min}$  by looking at the maximum value of the current  $I_{max}$ , a minimum time  $t_{min}$  and the maximum allowed voltage  $V_{CS}$ .  $C_{min}$  will therefore be expressed as

$$C_{min} = \frac{I_{max} t_{min}}{V_{CS, max}} \quad (27)$$

We will then have the restrictions

$$C_{min} \leq C_S \leq C_{max} \quad (28)$$


---

---

for  $C_S$ , where we can give the capacitors any given value within this range.

## 2.2 Digital part

To make the analog circuit work, we have to send in the control signals. In Figure 5 we can see the timing diagram including the different control signals in the circuit shown in Figure 2. The first signal shown in the diagram is *Clk*, which operates as the system clock. The signal *Init* turns high when we want to start the process of taking a picture with our digital camera, and will only be high for a single clock period. *Erase* starts high since we want  $C_S$  to be free from any charge when starting the exposure. After *Erase* turns low when *Init* turns low, *Expose* turns high. This results in the charging of  $C_S$ . After the expose time has passed, the overflow flag *Ovf5* turns high, which leads to *NRE\_R1* to turn low a clock period later. One clock period later, *ADC* goes from being low to high in a single clock period before going back to being low. *NRE\_R1* lasts for three clock periods, before turning back to high. When *NRE\_R1* turns high again, the overflow flag *Ovf4* turns high for a single clock period, which turns *NRE\_R2* to low a clock period later. Equal to *NRE\_R1*, *NRE\_R2* will last for three clock periods. A single clock period after *NRE\_R2* turns to low, *ADC* turns high again for one clock period. When *NRE\_R2* goes back to being high, *Ovf4* turns high for a clock period, which sends the camera back to Idle. When *NRE\_R1* or *NRE\_R2* is low we'll get an analog signal at the output *OUT* shown in Figure 2. *ADC* activates a clock period after a read signal and is only active for a single clock period because the voltage  $V_{OUT}$  needs to be stable for us to convert it to a digital signal.

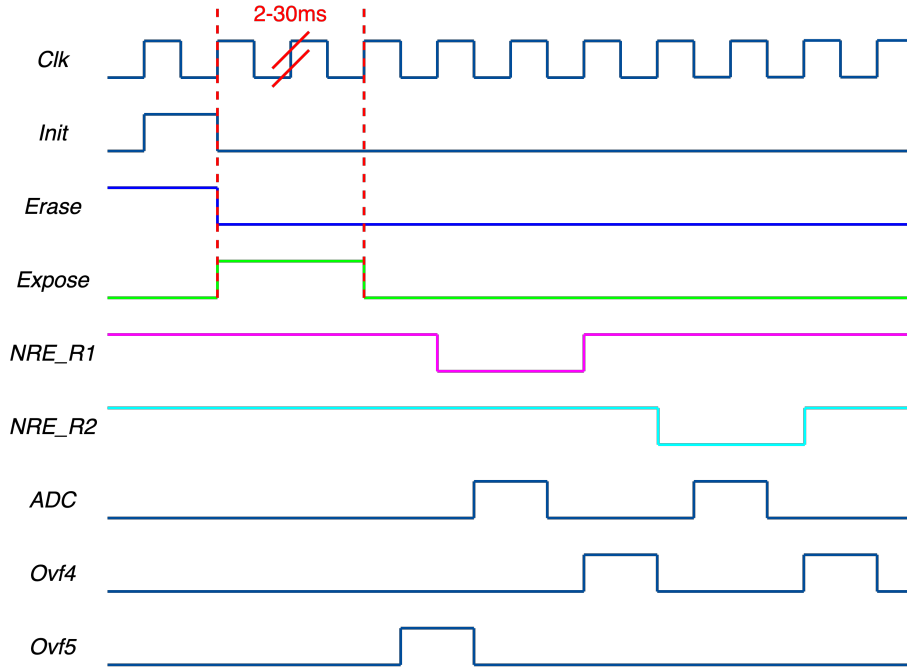


Figure 5: Overview of the timing diagram.

To create these digital control signals, we have to design a digital circuit. In Figure 6 we see a simplified version of the digital circuit's finite state machine (FSM). By implementing the system as an FSM, we can easily send out different signals based on different conditions.

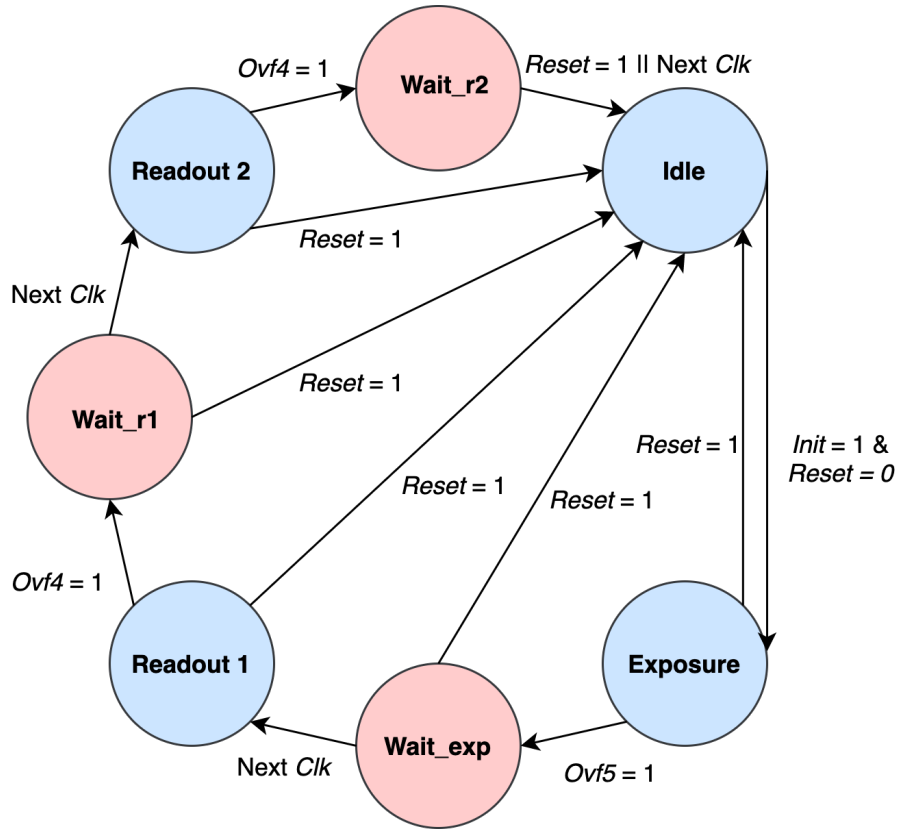


Figure 6: Overview of the FSM.

Initially, the FSM is in the state **Idle**. After the signal *Init* has been sent into the machine, it goes into the state **Exposure**. If *Reset* is high, it should stay in **Idle**, and also return to **Idle** if it is in any other state. After a certain amount of clock cycles determined by the signal *Clk*, the flag *Ovf5* is set to high. By waiting a bit after the exposure has started, we ensure that the capacitor  $C_S$  is fully charged. When *Ovf5* is set to high, the FSM enters a wait state **Wait\_exp** that lasts for one clock period. After this clock period, we enter the state **Readout 1** and *Ovf5* is set to low. Three clock cycles later, the overflow signal *Ovf4* will be set to high and the FSM enters the state **Wait\_r1**. This state lasts for one clock period and sends the FSM to **Readout 2** and sets *Ovf4* to low. After three clock periods, *Ovf4* is set to high again and the FSM enters the next state, **Wait\_r2**. As all the other wait states, **Wait\_r2** lasts for one clock period before going over to the next state **Idle** and setting *Ovf4* to low. The system will now remain idle or run another exposure. A more technical overview of the digital circuitry is shown in Figure 7.

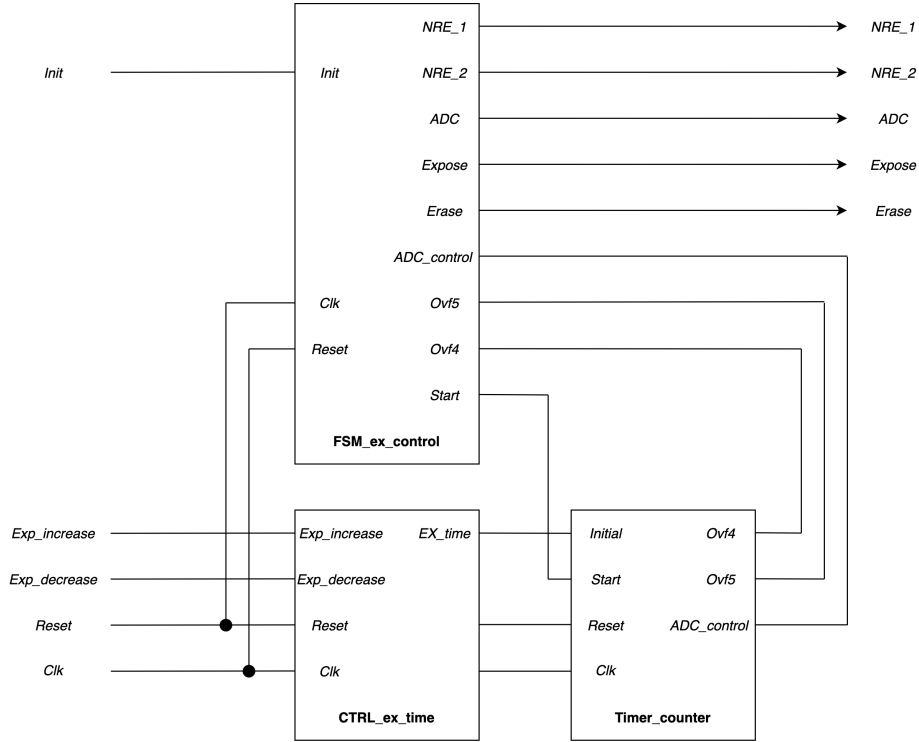


Figure 7: Overview of the block diagram for RE\_Control

We see that the digital circuit is composed of three smaller subcircuits, **FSM\_ex\_control**, **CTRL\_ex\_time** and **Timer\_counter**. In total, there are five input signals to the digital circuit **RE\_control**, being *Init*, *Exp\_increase*, *Exp\_decrease*, *Clk* and *Reset*. These are all external signals. As explained earlier, *Init* initiates the digital circuit, *Reset* resets the circuit, *Clk* is a clock signal and *Exp\_increase* and *Exp\_decrease* increases or decreases the exposure time. The function of the **CTRL\_ex\_time** block is to adjust the exposure- and read-time, which correlates to the *Expose*, *NRE\_1* and *NRE\_2* signals respectively. By adjusting *Exp\_increase* and *Exp\_decrease*, we adjust the *EX\_time* signal, which stands for exposure-time. The **Timer\_counter** box controls when we send out the overflow signal *Ovf5* and the control signal *ADC\_control*, by taking in *EX\_time*, *Start*, *Clk* and *Reset* as inputs. *Ovf5* is then being sent as an input to the **FSM\_ex\_control** subcircuit, which will then send out the wanted control signals to the analog circuit, being *NRE\_R1*, *NRE\_R2*, *ADC*, *EXPOSE* and *ERASE*. The *ADC\_control* signal controls when *ADC* should be high and when it should be low. The inputs of the **FSM\_ex\_control** subcircuit are *Init*, *Clk*, *Reset*, *Ovf5* and *ADC\_control* signals. When the digital circuit is implemented with the analog circuit, we will have a complete circuit looking like the block diagram in Figure 8.

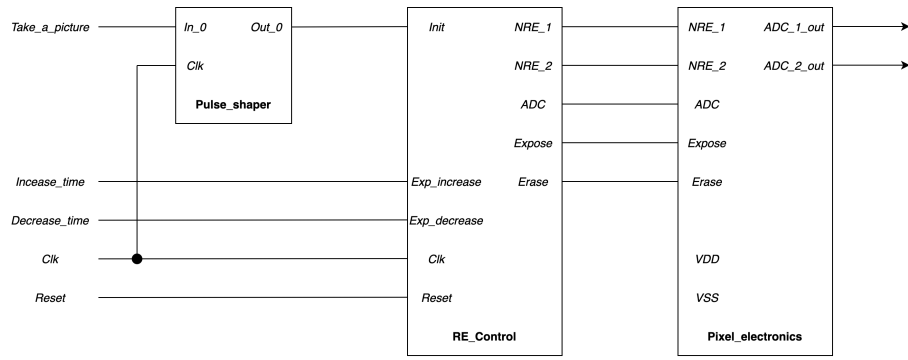


Figure 8: Overview of the block diagram for the entire camera circuit, composed of a **Pulse\_shaper**, the **RE\_Control** and the **Pixel\_electronics**. We are not going to design the **Puls\_shaper**.

Here we see the digital circuit's control signal outputs connected to the analog circuit, shown in Figure 3, represented as *RE\_Control* and *Pixel\_electronics*. The digital circuit shown in Figure 7 is represented as **RE\_Control**.

---

## 3 Realization

To simulate the digital camera, we use the circuit simulation program AIM-Spice for the analog part and the HDL Verilog in the simulation program Active HDL. This section will be divided in three parts: the calculation of parameters we use, how the AIM-Spice code is implemented and finally how the Verilog code is implemented.

### 3.1 Parameters

#### 3.1.1 Body effect parameters

In the model files, we have two different carrier concentrations  $N_A$ . We find that the carrier concentration  $N_{A,NMOS}$  is  $2.33 \cdot 10^{17}$  for the NMOS transistors and the carrier concentration  $N_{A,PMOS}$  is  $4.12 \cdot 10^{17}$  for the PMOS transistors. The thickness of the oxide layer  $t_{ox}$  is  $4.1 \cdot 10^{-9}$  cm for both the NMOS and PMOS transistors. The relative permittivity of silicon  $K_S$  is 11.8. The relative permittivity of SiO<sub>2</sub>  $K_{OX}$  is  $3.9 \text{Fm}^{-2}$ . The vacuum permittivity  $\epsilon_0$  is  $8.854 \cdot 10^{-12} \text{Fm}^{-1}$ . The elementary charge  $q$  is  $1.6 \cdot 10^{-19} \text{C}$ . By using (4) we get the gate capacitance  $C_{OX}$  to be approximately  $0.01 \text{Fm}^{-1}$ . By using the value we found for  $C_{OX}$  together with  $N_{A,NMOS}$ , the elementary charge  $q$ , the relative permittivity of silicon  $K_S$ , the vacuum permittivity  $\epsilon_0$  and by using (5), we find that  $\gamma_{NMOS}$  is approximately  $3.5 \cdot 10^{-4}$ . By switching  $N_{A,NMOS}$  with  $N_{A,PMOS}$ , we get that  $\gamma_{PMOS}$  is equal to approximately  $4.6 \cdot 10^{-4}$ . Since both  $\gamma_{NMOS}$  and  $\gamma_{PMOS}$  are extremely small, we can neglect the body effect.

#### 3.1.2 Transistor parameters

The transistor parameters have to be between the following values

$$0.36\mu m < L < 1.08\mu m \quad (29)$$

and

$$1.08\mu m < W < 5.04\mu m \quad (30)$$

Since we want the leakage current to be minimal in the transistors  $M1$  and  $M2$ , we set  $L_{M1}$  and  $L_{M2}$  to be maximal  $1.07\mu m$  and the widths  $W_{M1}$  and  $W_{M2}$  to be  $1.09\mu m$ . Since we want the transistors  $M4$  to have minimal impact on the buffers, we minimize the length  $L_{M4}$  to  $0.37\mu m$  and maximize the width  $W_{M4}$  to  $5.03\mu m$ . To maximize the gain on the voltage in  $OUT$ , we will have to set the length  $L_{M3}$  to a minimum of  $0.37\mu m$  and the length  $L_{MC}$  to a maximum of  $1.07\mu m$ , as well as setting the width  $W_{M3}$  to a maximum of  $5.03$  and the width  $W_{MC}$  to a minimum of  $1.09\mu m$ . These parameters are shown in table 1 in subsubsection 3.1.4.

#### 3.1.3 Capacitor parameters

The capacitors  $C_S$  parameters have to be under the following value

$$C_S \leq 3pF \quad (31)$$

and the capacitors  $C_{C1}$  and  $C_{C2}$  in the active loads have the given value

$$C_{C1} = C_{C2} = 3pF \quad (32)$$



---

The current  $I(\tau)$  is expected to be between the following values

$$50pA \leq I(\tau) \leq 750pA \quad (33)$$

and the exposure time has to be between

$$2ms \leq t \leq 30ms \quad (34)$$

The threshold voltage for the PMOS transistors is 0.39V and the supply voltage  $V_{DD}$  is 1.8V. By knowing this, we can use (12) and (13) to find that the maximum voltage  $V_{N2}$ , which is the same as  $V_{CS}$ , has to be lower than 1.02V. We will therefor set  $V_{CS,max}$  to be 1V. To calculate the minimum value for  $C_S$ , we have to insert the maximum voltage  $V_{CS,MAX}$ , maximum current  $I_{max}(\tau)$ , which is 750pA, and the minimum time  $t_{min}$ , which is 2ms, into (26). We the get the following restriction to the capacitors  $C_S$

$$1.5pF \leq C_S \leq 3pF \quad (35)$$

We will therefore choose the capacitors  $C_S$  to have a capacitance of 2.75F, since this is in the middle of the two values. These parameters are shown in table 1 in subsubsection 3.1.4.

#### 3.1.4 Parameters summary

The entire overview of the parameters of the components that we will implement in our analog circuit is shown in the table 1.

Parameter	Parameter value
$L_{M1}$	$1.07\mu m$
$L_{M2}$	$1.07\mu m$
$L_{M3}$	$0.37\mu m$
$L_{M4}$	$0.37\mu m$
$L_{MC}$	$1.07\mu m$
$W_{M1}$	$1.09\mu m$
$W_{M2}$	$1.09\mu m$
$W_{M3}$	$5.03\mu m$
$W_{M4}$	$5.03\mu m$
$W_{MC}$	$1.09\mu m$
$C_S$	$2.75pF$
$C_1$	$3pF$
$C_2$	$3pF$

Table 1: Table of transistor and capacitor parameters.

## 3.2 Analog circuitry

A premade test bench was used in the testing, as shown in the code. We implement the pixel circuits and the active loads by making two sub circuits containing the needed components. We can then create the four pixel circuits and two active loads in the configuration shown in Figure 3. We can then simulate the entire circuit with the test bench. The results from the simulation are shown in Figure 9.

 


Figure 9: The voltages of the signals *Expose*, *Erase*, *NRE\_R1*, *NRE\_R2*, the here identical output signals, and the voltage over  $C_S$ .

We can see that the *EXPOSE* signal enables the capacitors  $C_S$  to charge up and that the *ERASE* signal enables the capacitors  $C_S$  to discharge. We can also see that the *OUT* signal depends on the capacitor  $C_S$  when the *NRE\_R1* or *NRE\_R2* signal is active. In figure Figure 10 we see a worst case scenario with parameter variations that result in a slower digital circuit. This does not change the ideal output signal that much as we see when comparing Figure 9 wit Figure 10.

 


Figure 10: The voltages of the signals simulated with slow corners.

In figure Figure 10 we see a worst case scenario with parameter variations that result in a faster digital circuit. This changes the output signal by such a large amount that it would not operate as expected. We can clearly see this by comparing Figure 9 with Figure 11.

 


Figure 11: The voltages of the signals simulated with fast corners.

### 3.3 Digital circuitry

We implement the digital circuit by making each digital component shown in Figure 7. This is shown in the code as `FSM_ex_control`, `CTRL_ex_time` and `Timer_counter` in the Verilog code. The control signals are shown in Figure 12. The *Expose* signal is set to be 3ms in this instance. We can see that the signals look like in Figure 5.

 


Figure 12: Overview of the timing simulated control signals.

The *Exp\_increase* and *Exp\_decrease* signals work as well. This is shown in Figure 13, where we start with an exposure time of 3ms and decrease it over two clock periods until it is at the lower limit of 2ms.

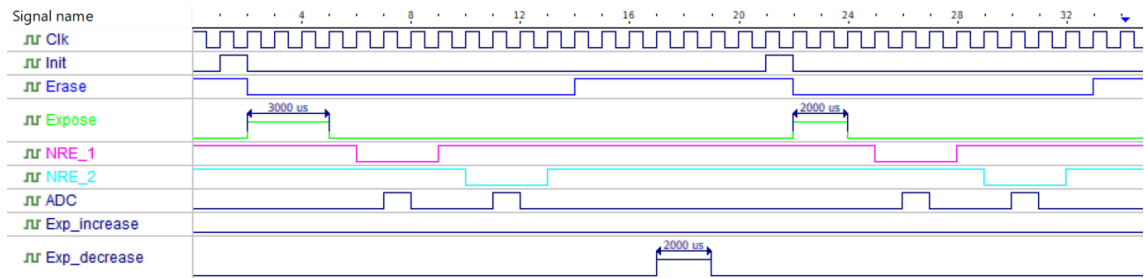


Figure 13: Overview of the timing diagram when decreasing time.

The reset signal works as shown in Figure 14. Here we see that the *reset* signal is set to high and that the digital control logic goes back to Idle. We then see that the digital control signals start again when we set the *Init* signal to high.

 


Figure 14: Overview of the timing diagram when resetting the signal.

---

## 4 Conclusion

We have designed both the analog part of the digital camera as well as the digital control logic. We implemented the analog circuitry in the simulator program AIM-spice. The digital control logic was implemented using Verilog in Active HDL. This resulted in a fully functional analog circuit with the correct digital control signals.

---

## Bibliography

- Carusone, Tony Chan, David A. Johns and Kenneth W. Martin (2012). *Analog Integrated Circuit Design*. WILEY.
- Larsen, Bjørn B. (2020). *TFE4152 - Design of integrated circuits 2020, Project description, Digital camera*. URL: [https://drive.google.com/file/d/1TBPxhWup2TgUld\\_N7HUfzBDP56rRkvY5/view?usp=sharing](https://drive.google.com/file/d/1TBPxhWup2TgUld_N7HUfzBDP56rRkvY5/view?usp=sharing) (visited on 16th Nov. 2020).
- NTNU, Department of Marine Technology (2020). *IMT Software Wiki - LaTeX*. URL: <https://www.ntnu.no/wiki/display/imtsoftware/LaTeX> (visited on 15th Sept. 2020).

---

# Appendix

## A AIM-Spice code

Project code

```
.include p18_model_card.inc
.include p18_cmos_models_tt.inc

* Photo Diode handout *

.subckt PhotoDiode VDD N1_R1C1
    I1_R1C1 VDD N1_R1C1 DC Ipd_1 ! Photo current source
    d1 N1_R1C1 VDD dwell 1 ! Reverse biased Diode
    .model dwell d cj0=1e-14 is=1e-12 m=0.5 bv=40 ! Diode model
    Cd1 N1_R1C1 VDD 30f! Photo diode capacitor
.ends

* Parameters *

.param L_M1 = 1.07u
.param W_M1 = 1.09u
.param L_M2 = 1.07u
.param W_M2 = 1.09u
.param L_M3 = 0.37u
.param W_M3 = 5.03u
.param L_M4 = 0.37u
.param W_M4 = 5.03u

.param L_MC = 1.07u      ! L_MC1 = L_MC2
.param W_MC = 1.09u      ! W_MC2 = W_MC2

.param CS_C = 2.75p
.param CC_C = 3p

* Test bench handout *

.param Ipd_1 = 50p ! Photodiode current, range [50 pA, 750 pA]
.param VDD = 1.8 ! Supply voltage
.param EXPOSURETIME = 2m ! Exposure time, range [2 ms, 30 ms]

.param TRF = {EXPOSURETIME/100} ! Risetime and falltime of EXPOSURE and ERASE
↪ signals
.param PW = {EXPOSURETIME} ! Pulsethickness of EXPOSURE and ERASE signals
.param PERIOD = {EXPOSURETIME*10}! Period for testbench sources
.param FS = 1k; ! Sampling clock frequency
.param CLK_PERIOD = {1/FS} ! Sampling clock period
.param EXPOSE_DLY = {CLK_PERIOD} ! Delay for EXPOSE signal
.param NRE_R1_DLY = {2*CLK_PERIOD + EXPOSURETIME} ! Delay for NRE_R1 signal
.param NRE_R2_DLY = {4*CLK_PERIOD + EXPOSURETIME} ! Delay for NRE_R2 signal
.param ERASE_DLY = {6*CLK_PERIOD + EXPOSURETIME} ! Delay for ERASE signal

VDD VDD 0 dc VDD
VEXPOSE EXPOSE 0 dc 0 pulse(0 VDD EXPOSE_DLY TRF TRF EXPOSURETIME PERIOD)
VERASE ERASE 0 dc 0 pulse(0 VDD ERASE_DLY TRF TRF CLK_PERIOD PERIOD)
VNRE_R1 NRE_R1 0 dc 0 pulse(VDD 0 NRE_R1_DLY TRF TRF CLK_PERIOD PERIOD)
VNRE_R2 NRE_R2 0 dc 0 pulse(VDD 0 NRE_R2_DLY TRF TRF CLK_PERIOD PERIOD)
```

---

```

* Pixel Circuit *

.subckt PixelCircuit VDD VSS EXPOSE ERASE NRE OUT N2
    XPD1 VDD N1 PhotoDiode

    M1 N1 EXPOSE N2 VSS NMOS L=L_M1 W=W_M1
    M2 N2 ERASE VSS VSS NMOS L=L_M2 W=W_M2
    M3 VSS N2 N3 VDD PMOS L=L_M3 W=W_M3
    M4 N3 NRE OUT VDD PMOS L=L_M4 W=W_M4

    CS N2 VSS CS_C
.ends

* Active Load *

.subckt ActiveLoad VDD VSS OUT
    MC OUT OUT VDD VDD PMOS L=L_MC W=W_MC

    CC OUT VSS CC_C
.ends

* Camera Circuit *

XPixel_1_1 VDD 0 EXPOSE ERASE NRE_R1 OUT1 N2 PixelCircuit
XPixel_2_1 VDD 0 EXPOSE ERASE NRE_R2 OUT1 N2 PixelCircuit
XPixel_1_2 VDD 0 EXPOSE ERASE NRE_R1 OUT2 N2 PixelCircuit
XPixel_2_2 VDD 0 EXPOSE ERASE NRE_R2 OUT2 N2 PixelCircuit
XActiveLoad_1 VDD 0 OUT1 ActiveLoad
XActiveLoad_2 VDD 0 OUT2 ActiveLoad

* Plot *

.plot V(N2) V(EXPOSE) V(ERASE) V(NRE_R1) V(NRE_R2) V(OUT1) V(OUT2)

```



---

## B Verilog code

```
`timescale 1ms / 1ps

module FSM_ex_control (
    input logic Clk,
    input real Clk_half_period,
    input logic Reset,
    input logic Init,
    input logic Ovf4,
    input logic Ovf5,
    input reg [4:0] Exp_time,
    input logic ADC_control,
    output logic NRE_1,
    output logic NRE_2,
    output logic ADC,
    output logic Expose,
    output logic Erase,
    output logic Start
);

typedef enum logic [2:0] { Idle, Exposure, Readout1, Readout2, Wait_exp,
    → Wait_r1, Wait_r2 } State;

State currentState, nextState;

always_ff @(posedge Clk) begin
    currentState = nextState;
end

always@(*) begin
    ADC = ADC_control;

    case(currentState)
        Idle: if(Init && !Reset)
            nextState = Exposure;
        else
            nextState = Idle;
        Exposure: if (Reset)
            nextState = Idle;
        else if (Ovf5)
            nextState = Wait_exp;
        else
            nextState = Exposure;
        Wait_exp: if (Reset)
            nextState = Idle;
        else begin
            #(2*Clk_half_period);
            nextState = Readout1;
        end
        Readout1: if(Reset)
            nextState = Idle;
        else if (Ovf4)
            nextState = Wait_r1;
        else
            nextState = Readout1;
        Wait_r1: if (Reset)
```

---

---

```

        nextState = Idle;
    else begin
        #(2*Clk_half_period);
        nextState = Readout2;
    end
Readout2: if (Reset)
    nextState = Idle;
else if(Ovf4)
    nextState = Wait_r2;
else
    nextState = Readout2;
Wait_r2: if (Reset)
    nextState = Idle;
else begin
    #(2*Clk_half_period);
    nextState = Idle;
end
default:
    nextState = Idle;
endcase
end

assign Expose = (currentState == Exposure);
assign Erase = (currentState == Idle);
assign NRE_1 = !(currentState == Readout1);
assign NRE_2 = !(currentState == Readout2);
assign Start = !(currentState == Idle);

endmodule

module CTRL_ex_time (
    input logic Clk,
    input logic Reset,
    input logic Exp_increase,
    input logic Exp_decrease,
    output reg [4:0] Exp_time
);

    initial
        Exp_time = 3;

    always @ (posedge Clk) begin
        if (Exp_increase && Exp_time < 30)
            Exp_time <= Exp_time+1;
        else if (Exp_decrease && Exp_time > 2)
            Exp_time <= Exp_time-1;
    end
endmodule

module Timer_counter(input logic Start,
    input logic Clk,
    input logic Reset,
    input reg [4:0] Initial,
    output logic Ovf4,
    output logic Ovf5,
    output logic ADC_control);

```

---

---

```

integer Exp_counter = 0;
integer Read_counter = 0;
logic Read_count1 = 0;
logic Read_count2 = 0;
integer Read_time = 3;

initial begin
    Ovf4 = 0;
    Ovf5 = 0;
end

always_comb begin
    if ((Read_count1 || Read_count2) && Read_counter == 3 && Start)
        ADC_control = 1;
    else
        ADC_control = 0;
end

always @(posedge Clk) begin
    if ((Ovf5 || Read_count1) && Start) begin
        if (Start && (Read_counter < Read_time)) begin
            Read_counter = Read_counter + 1;
            Read_count1 = 1;
            Ovf5 = 0;
        end
        else if (Start && (Read_counter == Read_time)) begin
            Ovf4 = 1;
            Read_counter = 0;
            Read_count1 = 0;
        end
    end
    else if (Start && (Ovf4 || Read_count2)) begin
        if (Start && (Read_counter < Read_time)) begin
            Read_counter = Read_counter + 1;
            Read_count2 = 1;
            Ovf4 = 0;
        end
    end
    else if (Start && (Read_counter == Read_time)) begin
        Ovf4 = 1;
        Read_counter = 0;
        Read_count2 = 0;
    end
    else if (Start && (Exp_counter < Initial-2 && !Ovf4)) begin
        Exp_counter = Exp_counter + 1;
    end
    else if (Start && (Exp_counter == Initial-2 && !Ovf4)) begin
        Ovf5 = 1;
        Exp_counter = 0;
    end
    else begin
        Ovf4 = 0;
        Read_counter =
            ↪ 0;
        Read_count1 = 0;
        Read_count2 = 0;
    end
end

```

---

---

```
        end
endmodule
```

---

## C Verilog test bench

```
`timescale 1ms / 1ps

module system_testbench;

    logic Init, Exp_increase, Exp_decrease, Clk, Reset; // input
    logic NRE_1, NRE_2, ADC, Expose, Erase; //
    ⇨ output
    logic Ovf, Start;
    real Clk_half_period = 0.5;
    reg [4:0] Initial;

    always
        begin
            Clk <= 1; #Clk_half_period;
            Clk <= 0; #Clk_half_period;
        end

    FSM_ex_control dut_FSM(
        .Clk(Clk),
        .Clk_half_period(Clk_half_period),
        .Reset(Reset),
        .Init(Init),
        .Ovf4(Ovf4),
        .Ovf5(Ovf5),
        .ADC_control(ADC_control),
        .Exp_time(Initial),
        .NRE_1(NRE_1),
        .NRE_2(NRE_2),
        .ADC(ADC),
        .Expose(Expose),
        .Erase(Erase),
        .Start(Start));

    CTRL_ex_time dut_CTRL_ex_time(
        .Clk(Clk),
        .Reset(Reset),
        .Exp_increase(Exp_increase),
        .Exp_decrease(Exp_decrease),
        .Exp_time(Initial));

    Timer_counter dut_Timer(
        .Start(Start),
        .Clk(Clk),
        .Reset(Reset),
        .Initial(Initial),
        .Ovf4(Ovf4),
        .Ovf5(Ovf5),
        .ADC_control(ADC_control));

    initial
        begin
```

---

```
Reset <= 1; Init <= 0; Exp_increase <= 0; Exp_decrease <=
→ 0; #(2*Clk_half_period);

Reset <= 0; Init <= 1; #(2*Clk_half_period);

Init <= 0; #(14*Clk_half_period);

end

endmodule
```